

### Aufgabe 3.1


a)  $i_0 = \frac{U_q}{2R} = 0,75 \text{ A}$  ,  $q_\infty = C U_q = 1,5 \text{ C}$

b)  $q(t) = C U_q (1 - e^{-t/(2RC)})$  ,  $i(t) = \dot{q}(t) = \frac{U_q}{2R} e^{-t/(2RC)}$

$$q(t_1) = C U_q (1 - e^{-t_1/(2RC)}) = \frac{3}{4} C U_q \Rightarrow t_1 = -2RC \ln\left(\frac{1}{4}\right) \approx 2,77 \text{ s}$$

$$i(t_1) = \frac{U_q}{2R} e^{-t_1/(2RC)} = \frac{1}{4} \cdot \frac{U_q}{2R} = 0,1875 \text{ A}$$

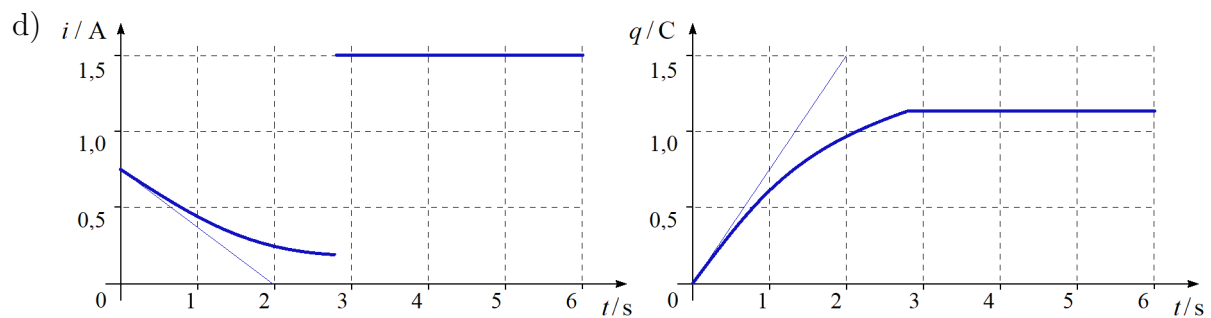c)  $i_2 = \frac{U_q}{R} = 1,5 \text{ A}$  ,  $q_2 = q(t_1) = \frac{3}{4} C U_q = 1,125 \text{ C}$



### Aufgabe 3.2

a)  $\underline{Z} = \underline{Z}_L + \underline{Z}_{RC}$  ,  $\underline{Z}_L = j\omega L$  ,  $\frac{1}{\underline{Z}_{RC}} = \frac{1}{R} + j\omega C$

$$\Rightarrow \underline{Z} = j\omega L + \frac{1}{1/R + j\omega C}$$

$$\Rightarrow \underline{Z} = j 200 \text{ s}^{-1} \cdot 1 \text{ H} + \frac{1}{1/500 \Omega + j 200 \text{ s}^{-1} \cdot 10^{-5} \text{ F}}$$

$$= j 200 \Omega + \frac{1}{0,002 + j 0,002} \Omega$$

$$= j 200 \Omega + \frac{0,002 - j 0,002}{0,002^2 + 0,002^2} \Omega$$

$$= j 200 \Omega + 250 \Omega - j 250 \Omega = 250 \Omega - j 50 \Omega$$

$$\underline{u} = \underline{Z} \underline{i} = (250 \Omega - j 50 \Omega) \cdot 0,1 \text{ A} = 25 \text{ V} - j 5 \text{ V}$$

$$\Rightarrow \hat{u} = |\underline{u}| = \sqrt{25^2 + 5^2} \text{ V} = 5\sqrt{26} \text{ V} \approx 25,5 \text{ V}$$

$$\Delta\varphi = \tan^{-1}\left(\frac{\Re(\underline{Z})}{\Im(\underline{Z})}\right) = \tan^{-1}\left(\frac{-5}{25}\right) = \tan^{-1}\left(-\frac{1}{5}\right) \approx -11,3^\circ$$

b)

